
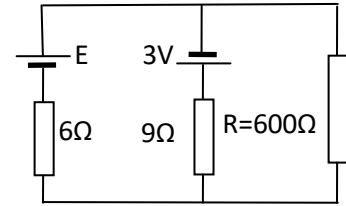


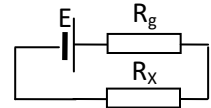1. U kolu na slici odrediti E tako da kroz otpornik R ne protiče struja.



2. U kolu na slici odrediti otpornost R_x tako da se na njemu razvija maksimalna snaga i odrediti tu snagu. Poznato je: $R_g=1\Omega$, $E=12V$.




3. Kolika količina elektriciteta protekne kroz konturu električne otpornosti $3,14\Omega$, prečnika $0,6\text{mm}$ kada se okrene iz položaja maksimalnog u položaj nultof magnetnog fluksa u homogenom magnetnom polju indukcije $30\mu\text{T}$?
4. Otpornik otpornosti 300Ω , kalem induktivnosti L i kondenzator kapaciteta C vezani su redno. Pri merenju impedanse ove veze ustanovljeno je da je ona najmanja na frekvenciji od 300Hz . Odrediti induktivnost kabela i kapacitet kondenzatora ako je pri frekvenciji 500Hz impedansa kola 500Ω .

Rešenja

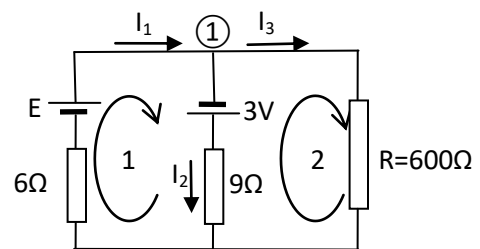1. Primenom Kirhofovih zakona imamo:

$$\left. \begin{array}{l} \text{Cvor 1} \quad I_1 - I_2 - I_3 = 0 \\ \text{Kontura 1} \quad 6I_1 + 9I_2 = E + 3 \\ \text{Kontura 2} \quad -9I_2 + 600I_3 = -3 \end{array} \right\}$$



$$\left. \begin{array}{l} 6(I_2 + I_3) + 9I_2 = E + 3 \\ -9I_2 + 600I_3 = -3 \end{array} \right\} \Rightarrow \left. \begin{array}{l} 15I_2 + 6I_3 = E + 3 \\ -9I_2 + 600I_3 = -3 \end{array} \right\} \Rightarrow I_3 = \frac{E-2}{1006} = 0 \Rightarrow E = 2V$$

$$2. P(R_x) = R_x I^2 = R_x \frac{E^2}{(R_g + R_x)^2} \quad \frac{dP}{dR_x} = 0 \Rightarrow \frac{d}{dR_x} (E^2 R_x (R_g + R_x)^{-2}) = 0$$

$$(R_g + R_x)^{-2} - 2R_x (R_g + R_x)^{-3} = 0 \Rightarrow R_x = R_g = 1\Omega, \quad P_{\max} = 1\Omega \frac{12^2}{2^2} W = 36W$$

$$3. e = -\frac{d\Phi}{dt} = -\frac{\Delta\Phi}{\Delta t} = -\frac{\Phi_2 - \Phi_1}{\Delta t} = \frac{\Phi_1 - \Phi_2}{\Delta t} \quad e = i \cdot R = \frac{\Delta q}{\Delta t} R = \frac{\Phi_1 - \Phi_2}{\Delta t} \Rightarrow \Delta q = \frac{\Phi_1 - \Phi_2}{R}, \quad \Phi_2 = 0$$


$$\Delta q = \frac{\Phi_1}{R} = \frac{B \cdot S}{R} = \frac{3 \cdot 10^{-5} T \cdot \pi \cdot (6 \cdot 10^{-4})^2 m^2}{4 \cdot 3,14 \Omega} = 2,7 \cdot 10^{-12} C$$

4. Impedansa je minimalna na rezonantnoj frekvenciji tj. kada je $L\omega - 1/C\omega = 0 \Rightarrow LC = \frac{1}{\omega_{rez}^2}$.


$$LC = \frac{1}{4\pi^2 \cdot 300^2} = 2,814477 \cdot 10^{-7} s^2 / rad^2. \quad Z = \sqrt{R^2 + X^2} \Rightarrow 500^2 = 300^2 + X^2 \Rightarrow X = L\omega - \frac{1}{C\omega} = \begin{cases} 400\Omega \\ -400\Omega \end{cases}$$

$$L\omega - \frac{1}{C\omega} = X \Rightarrow L = \frac{\omega X}{\omega^2 - \omega_{rez}^2} = \frac{2\pi \cdot f \cdot 400}{4\pi^2 (f^2 - f_{rez}^2)} = \frac{500 \cdot 400}{2\pi \cdot (500^2 - 300^2)} = 198,94 \cdot 10^{-3} H, \quad C = \frac{1}{L\omega_{rez}^2} = 1,41471 \cdot 10^{-6} F$$

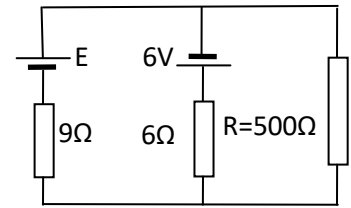1. U kolu na slici odrediti E tako da kroz otpornik R ne protiče struja.




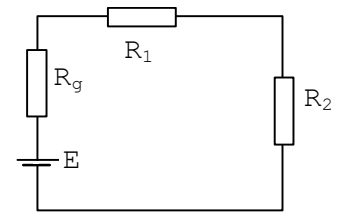2. U električnom kolu jednosmerne struje, prikazano na slici, odrediti vrednost otpornosti otpornika R_1 tako da snaga toplotnih gubitaka na ovom otporniku bude maksimalna. Poznate su sledeće vrednosti u kolu: $R_g=5\Omega$, $R_2=1000\Omega$.



3. Kolika je magnetna indukcija homogenog magnetnog polja ako kroz konturu električne otpornosti $6,28\Omega$, poluprečnika $0,2\text{mm}$ protokne količina elektriciteta $6,4\text{nC}$ kada se okrene iz položaja maksimalnog u položaj nultog magnetnog fluksa?

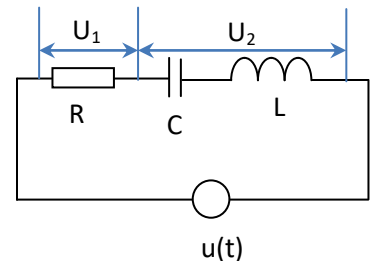
4. U kolu na slici priključen je naizmenični napon od 220V frekvencije 50Hz . Struja u kolu je 5A a napon $U_2 = \sqrt{3}U_1$. Odrediti R i U_2 .



Rešenja

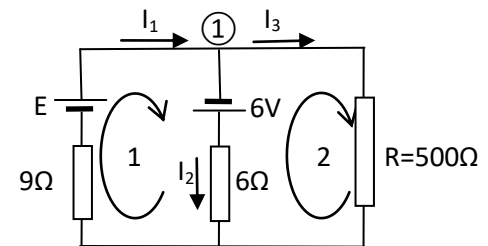1. Primenom Kirhofovih zakona imamo:

$$\left. \begin{array}{l} \text{Cvor 1} \quad I_1 - I_2 - I_3 = 0 \\ \text{Kontura 1} \quad 9I_1 + 6I_2 = E + 6 \\ \text{Kontura 2} \quad -6I_2 + 500I_3 = -6 \end{array} \right\}$$



$$\left. \begin{array}{l} 9(I_2 + I_3) + 6I_2 = E + 6 \\ -6I_2 + 500I_3 = -6 \end{array} \right\} \Rightarrow \left. \begin{array}{l} 15I_2 + 9I_3 = E + 6 \\ -6I_2 + 500I_3 = -6 \end{array} \right\} \Rightarrow I_3 = \frac{E - 9}{1259} = 0 \Rightarrow E = 9\text{V}$$

$$2. \quad I = \frac{E}{R_g + R_1 + R_2} = \frac{E}{1005 + R_1} \quad P_{R_1} = R_1 I^2 = R_1 \frac{E^2}{(1005 + R_1)^2} \cdot \text{Uslov ekstrema } \frac{dP_{R_1}}{dR_1} = 0$$

$$\frac{dP_{R_1}}{dR_1} = \frac{d}{dR_1} \left(E^2 R_1 (R_1 + 1005)^{-2} \right) = E^2 \left[(R_1 + 1005)^{-2} + R_1 (-2)(R_1 + 1005)^{-3} \right] = 0, \quad 2R_1 = R_1 + 1005 \Rightarrow R_1 = 1005\Omega$$

$$3. \quad e = -\frac{d\Phi}{dt} = -\frac{\Delta\Phi}{\Delta t} = -\frac{\Phi_2 - \Phi_1}{\Delta t} = \frac{\Phi_1 - \Phi_2}{\Delta t} \quad e = i \cdot R = \frac{\Delta q}{\Delta t} R = \frac{\Phi_1 - \Phi_2}{\Delta t} \Rightarrow \Delta q = \frac{\Phi_1 - \Phi_2}{R}, \quad \Phi_2 = 0$$

$$\Delta q = \frac{\Phi_1}{R} = \frac{B \cdot S}{R} \Rightarrow B = \frac{R \Delta q}{S} = \frac{6,28 \cdot 6,4 \cdot 10^{-9}}{\pi \cdot (2 \cdot 10^{-4})^2} = 0,3198\text{T}$$

$$4. \quad U^2 = U_1^2 + U_2^2 = U_1^2 + 3U_1^2 = 4U_1^2, \quad U_1 = U/2.$$

$$U_2 = \sqrt{3} \cdot 220/2 = 190,525\text{V}, \quad R = \frac{U_1}{I} = \frac{U}{2I} = \frac{220}{2 \cdot 5} \Omega = 22\Omega$$